

Roll No. ....

(05/16-I)

**5176**

**B.A./B.Sc. EXAMINATION**

(Second Semester)

COMPUTER SCIENCE

Second Paper

Logical Organisation of Computer

*Time : Three Hours    Maximum Marks :*  $\begin{cases} \text{B.Sc.: 30} \\ \text{B.A. : 20} \end{cases}$

**Note :** Attempt *one* question from each Unit. Q. No. 1 is compulsory. All questions carry equal marks. (For B.Sc. students, each question carries 6 marks and for B.A. students, each question carries 4 marks.)

1. **Note :** B.Sc. students attempt all the six parts in this question and B.A. students attempt any *four* parts. Each part carries 1 mark.

- (a) Explain the characteristics of sequential circuit.
- (b) Define flip-flop.
- (c) Define PIPO register.
- (d) Define flash memory.
- (e) Define preset and clear pulse in a flip-flop operation.
- (f) Define ROM.

#### Unit I

- 2. What do you mean by race around condition ? How does a master slave flip-flop overcome it ?
- 3. (a) Differentiate between combinational circuit and sequential circuit.
- (b) Define state table and state diagram using a suitable example.

#### Unit II

- 4. (a) Define counters and its various types.

- (b) Differentiate between synchronous and asynchronous counters.

- 5. What do you mean by shift register ? What are various other types of registers ?

#### Unit III

- 6. Write a note on SRAM, DRAM and ROM.
- 7. (a) What are various secondary storage memories ?
- (b) Differentiate between Cache memory and flash memory, random access memory and sequential access memory.

#### Unit IV

- 8. Define Bus and its types, various instruction types and instruction formats.
- 9. Write a detailed note on various data transfer modes.